

# **EMB3**

# **Advanced Programmable Electronics**

Lecture 2

Thursday, February

Jørgen Christian Larsen


[jcla@mmmi.sdu.dk](mailto:jcla@mmmi.sdu.dk)

# Lecture Overview

- FPGA internal layout
- Overall design guidelines
- Best practices
- Feedback on assignment
- Exercise
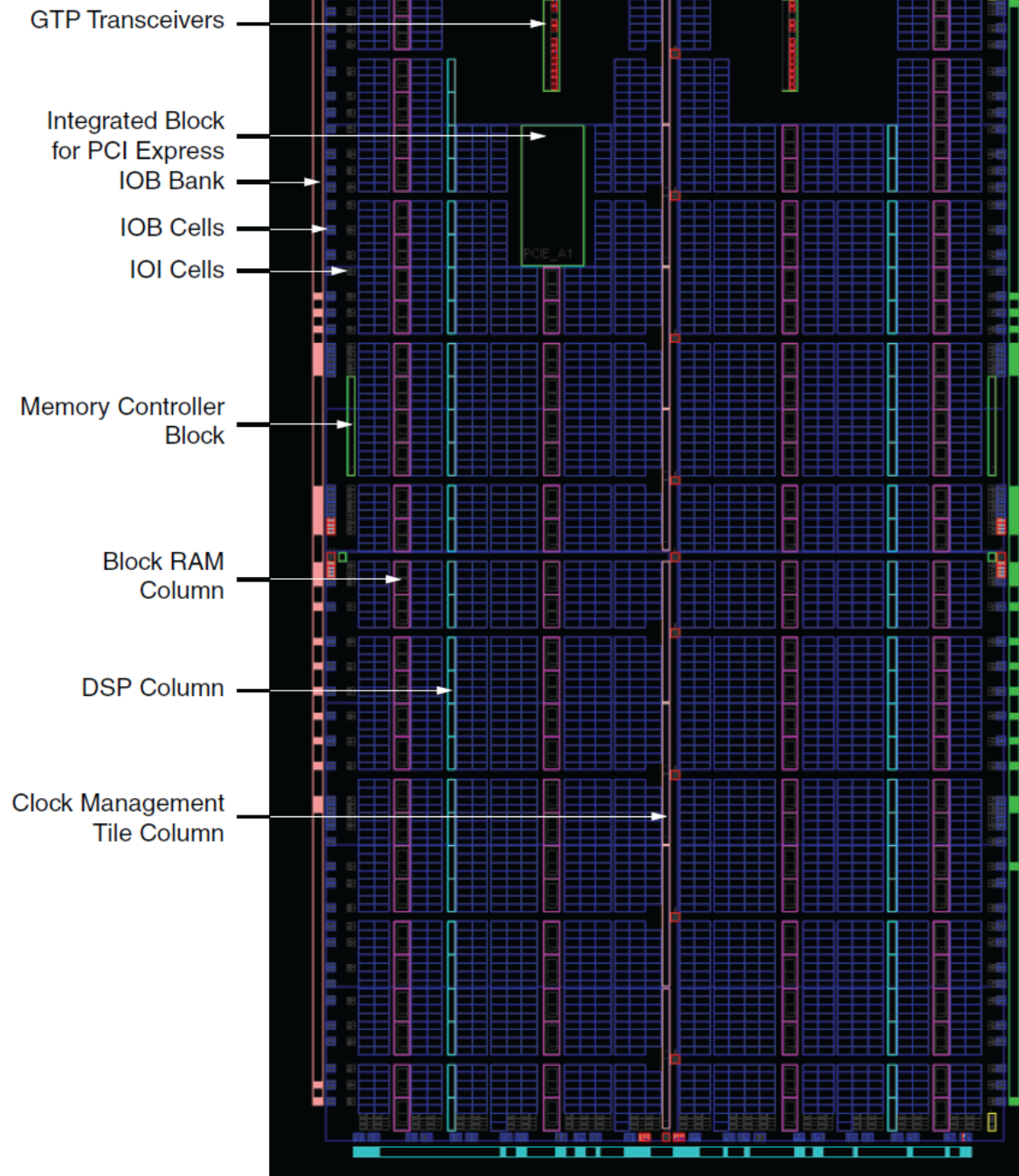
# FPGA internal layout

- Spartan-6 family architecture
  - 8 (9) fundamental programmable elements:
    - Configurable Logic Block (CLB)
    - Block RAM (BRAM)
    - Digital Signal Processing slice (DSP slice)
    - Input / Output Tile (IOT)
      - IOB + IOI
    - Clock Management Tile (CMT)
      - DCM + PLL
    - Memory Controller Block (MCB)
    - (LXT only) High Speed GTP serial transceiver (GTP)
    - (LXT only) Integrated PCI Express Endpoint block (PCIE)




# FPGA internal layout

- Spartan-6 family architecture (continued)
  - Distribution Networks
    - Signal Routing
    - Clock Routing

# FPGA internal layout

- Generalized Spartan 6 CLB

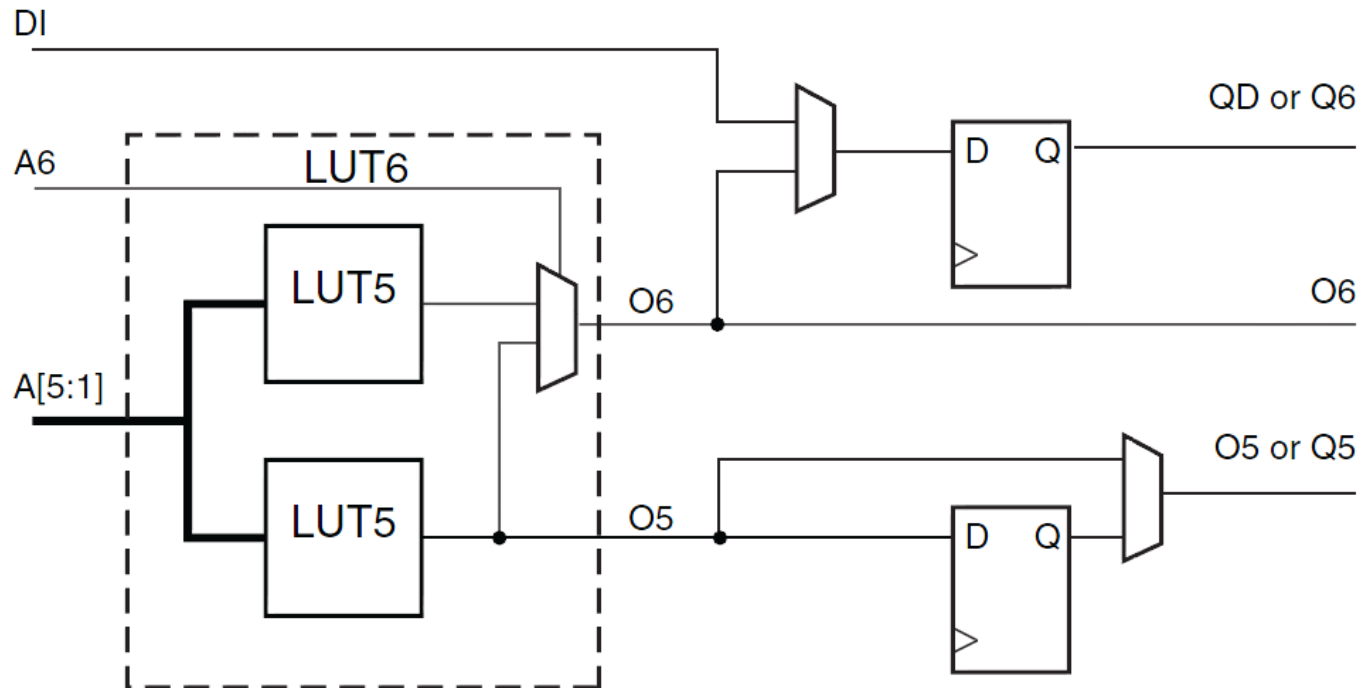


UG384\_06new\_021210

# FPGA internal layout
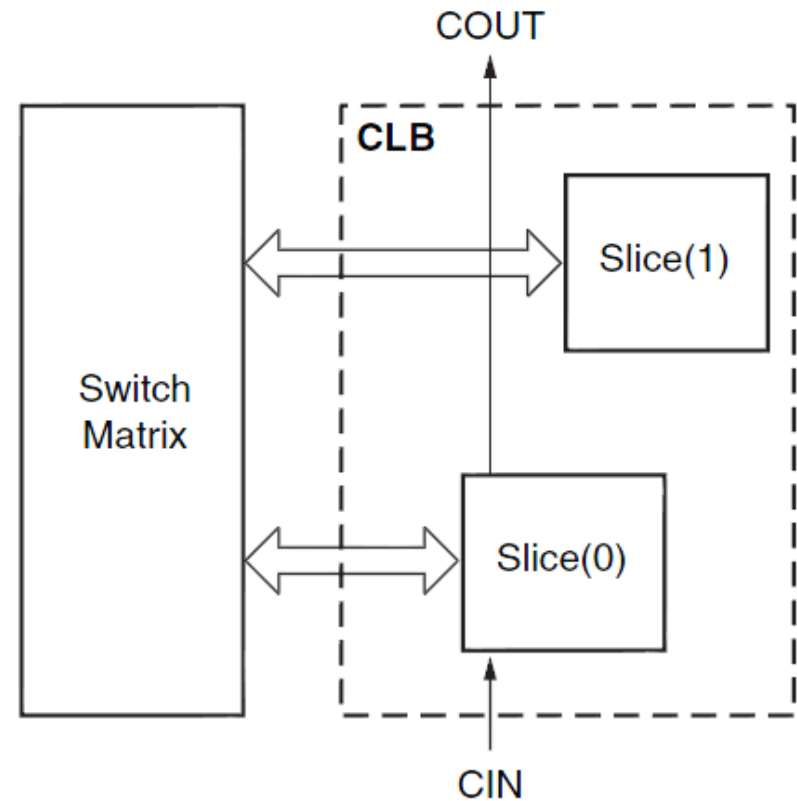
## Spartan 6 CLB slice's

- Each CLB contains 2 slices
- Each slice contains:
  - 4 6-input LUTS
    - Distributed RAM
    - Shift Registers
  - 8 Flip-Flops
  - Wide Multiplexers
  - Fast Carry Logic (only for slice 0 on Spartan-6)



ug384\_01\_042309

Figure 1: Arrangement of Slices within the CLB

# FPGA internal layout

- Spartan-6 CLB Storage elements
  - 4 Registers
  - 4 Register/Latch's
  - Reset Type
    - Sync
    - Async
  - Set, Reset, Init value
  - Clock, CE, Set/Reset

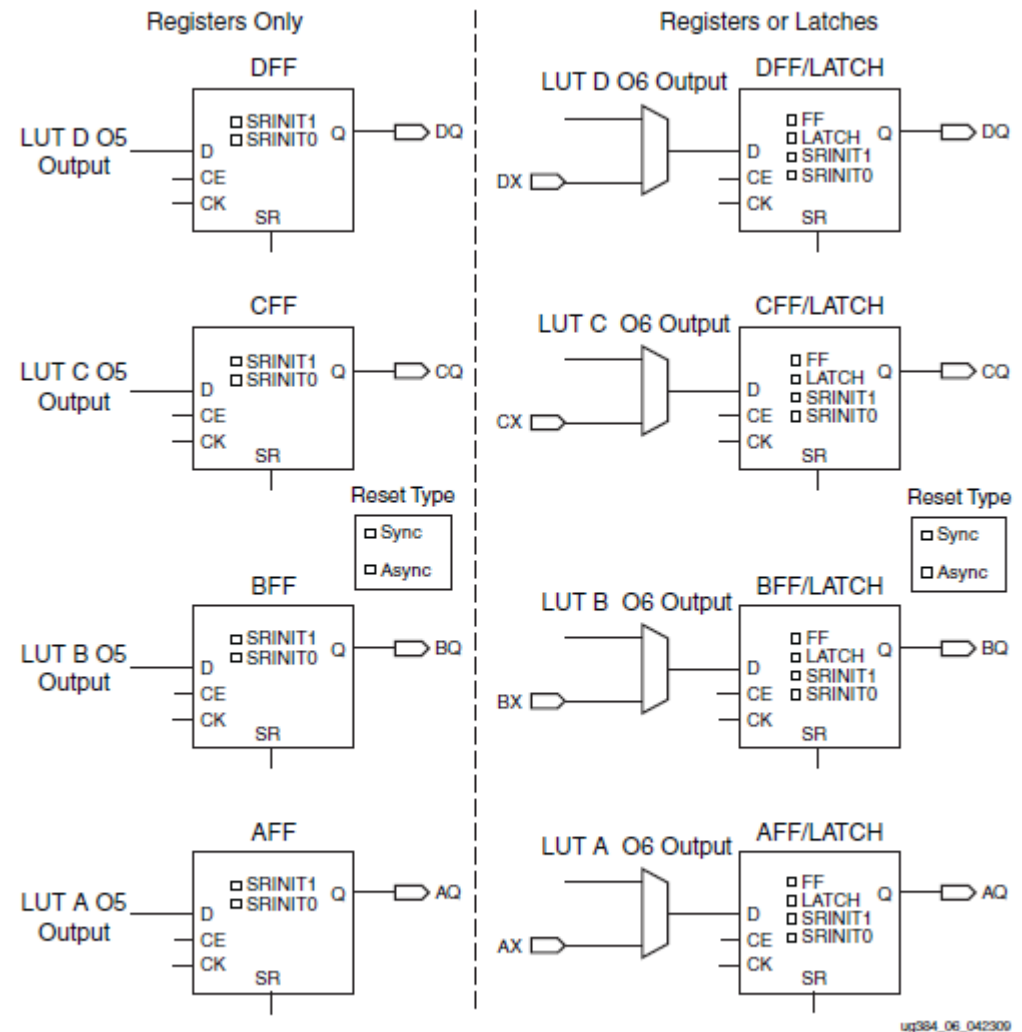



Figure 7: Configuration in a Slice: 4 Registers Only and 4 Register/Latch

ug384\_06\_042300


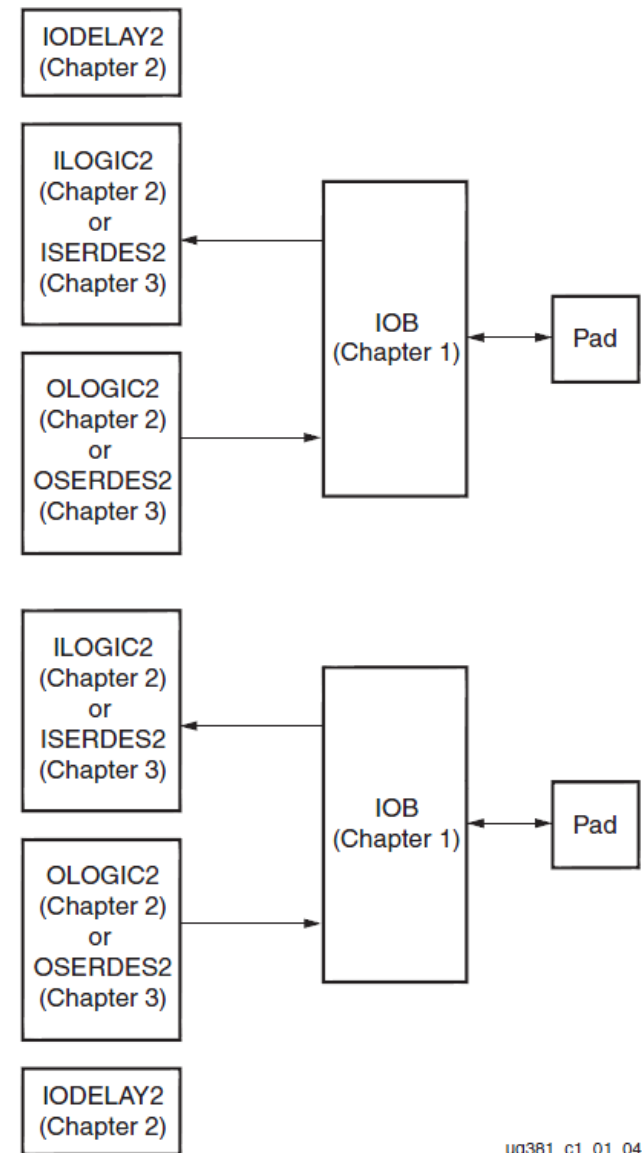
# FPGA internal layout

- Spartan-6 IO Tile
  - 1 pair/ 2 IO-Pads, IOB's, IOI's



ug381\_c1\_01\_041709

Figure 1-1: Spartan-6 FPGA I/O Tile

# FPGA internal layout

- IOB
  - IO-Mode: Input, Output, Tri-state
  - Drive Strength
  - Slew Rate
  - Termination
  - IO-Standard


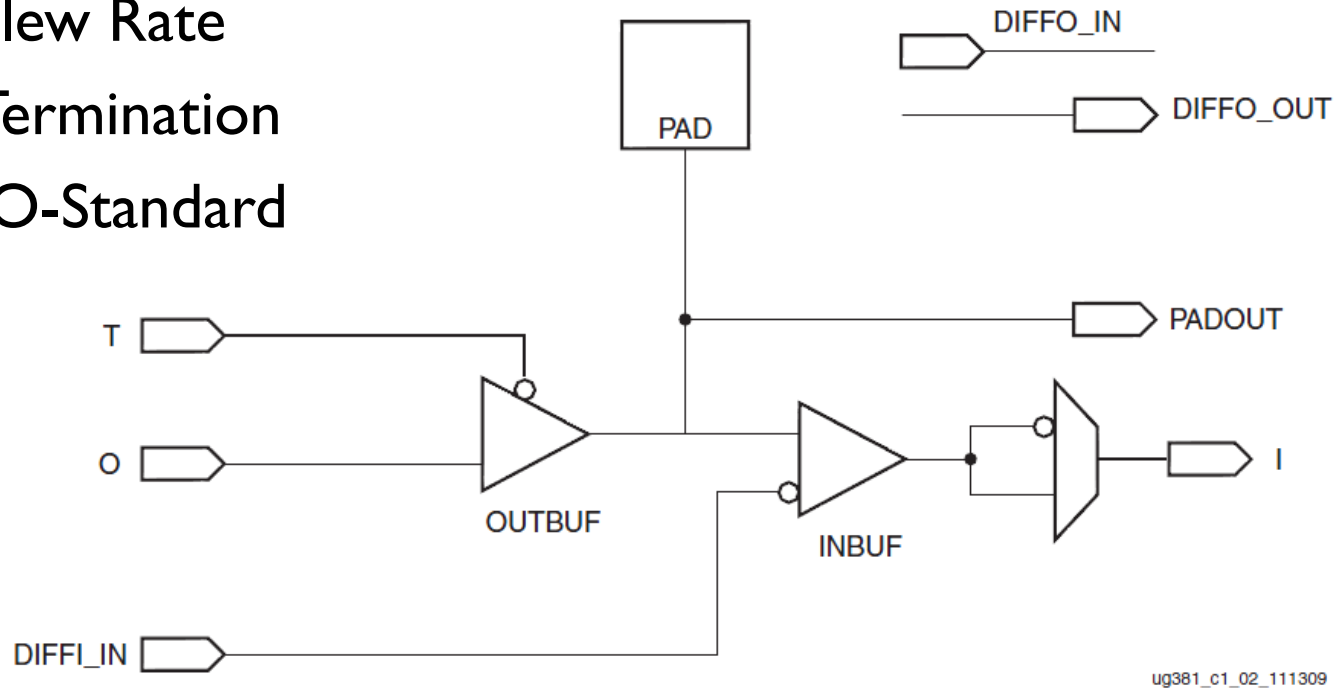


Figure 1-2: Basic IOB Diagram

 
# FPGA internal layout

- IO Banks
  - IO pads, IOB's and IOI's are grouped into Banks
  - Each Bank has a common set of  $V_{cco}$  Pins
    - Each IO pin in a given IO-Bank MUST share the same IO voltage  $V_{cco}$
    - Allows for easy glueless interfacing to several voltage standards

LX4, LX9, LX16, LX25, LX25T, LX45, LX45T  
and all devices in the 484-pin packages



 LX75, LX75T, LX100, LX100T, LX150, LX150T  
except devices in the 484-pin packages




ug381\_c1\_03\_111209

Figure 1-3: Spartan-6 FPGA I/O Banks
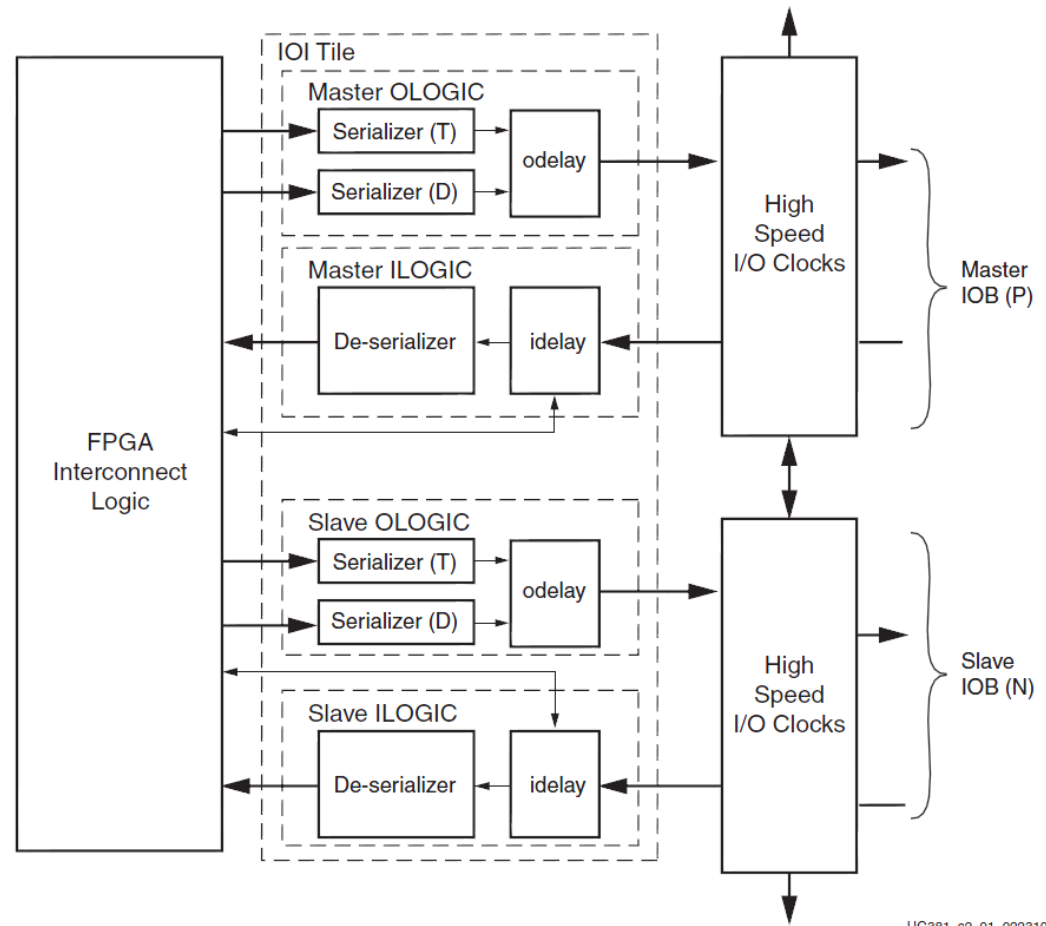
# FPGA internal layout

- IO Interface (IOI) tile
  - Can operate in
    - Parallel
    - Differential mode
- Adj. IO delay
- DDR I/O
- IO Serializer/De-Serializer
  - Up to 1080Mb/s
  - Single-ended  
1:1, 1:2, 1:3, 1:4
  - Differential  
1:5, 1:6, 1:7, 1:8




UG381\_c2\_01\_022310

Figure 2-1: SelectIO Logic Resources within the I/O Input Tile

# FPGA internal layout

## ■ Global Clock Distribution Network

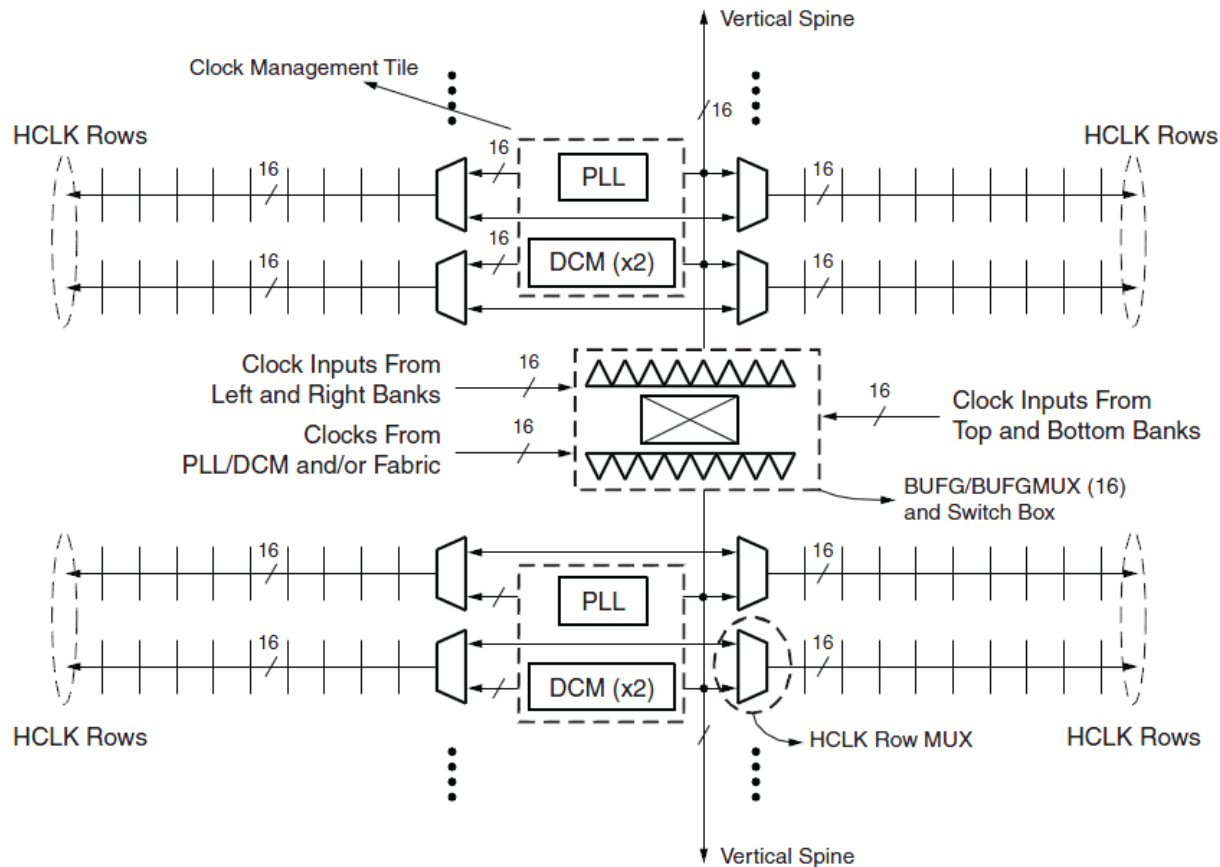


UG382\_c1\_01\_081009

Figure 1-1: Spartan-6 FPGA Global Clock Structure

# FPGA internal layout

- Global Clock Distribution Network

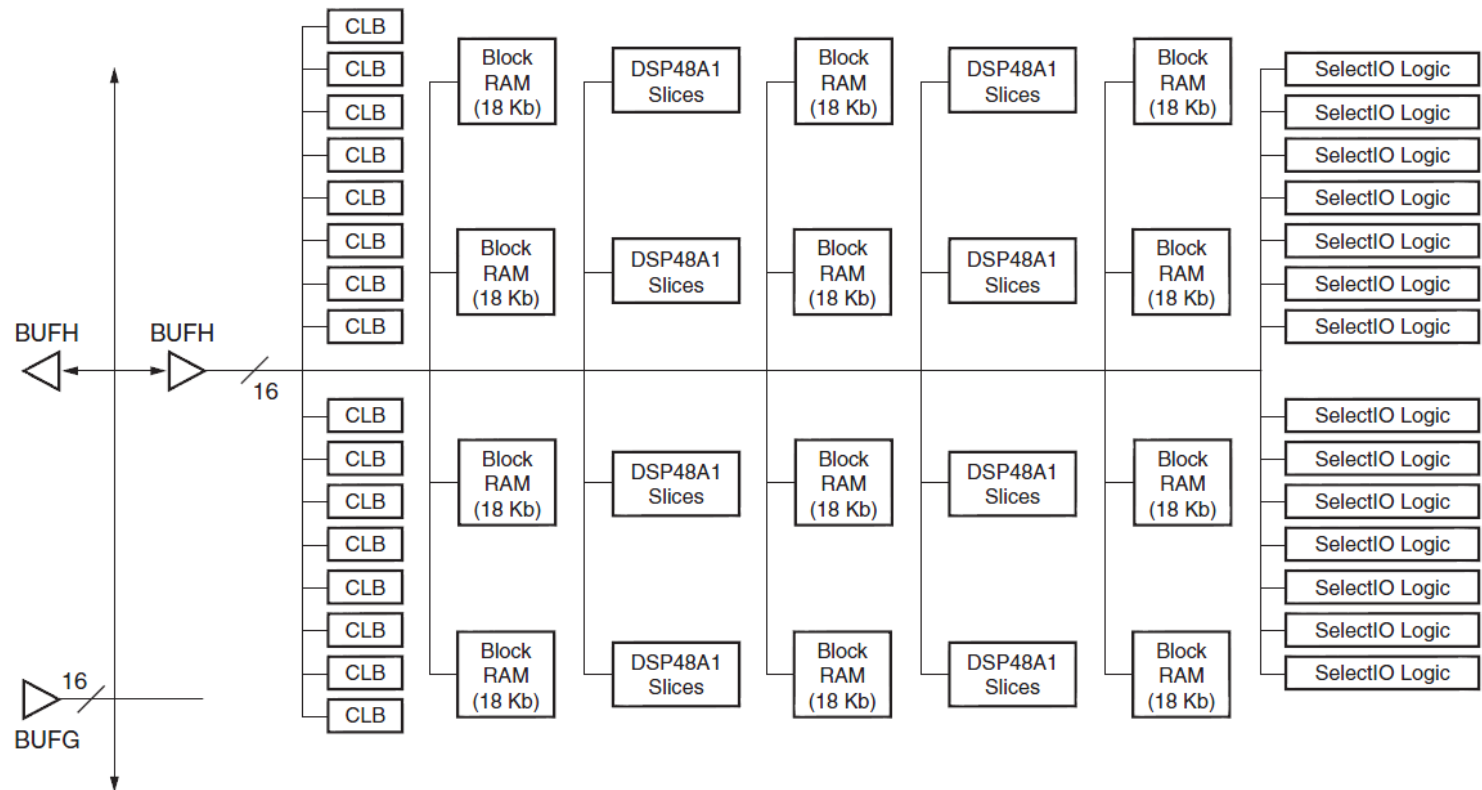


UG382\_c1\_02\_060410

Figure 1-2: BUFH Routing

# FPGA internal layout

- Interconnect Distribution Network

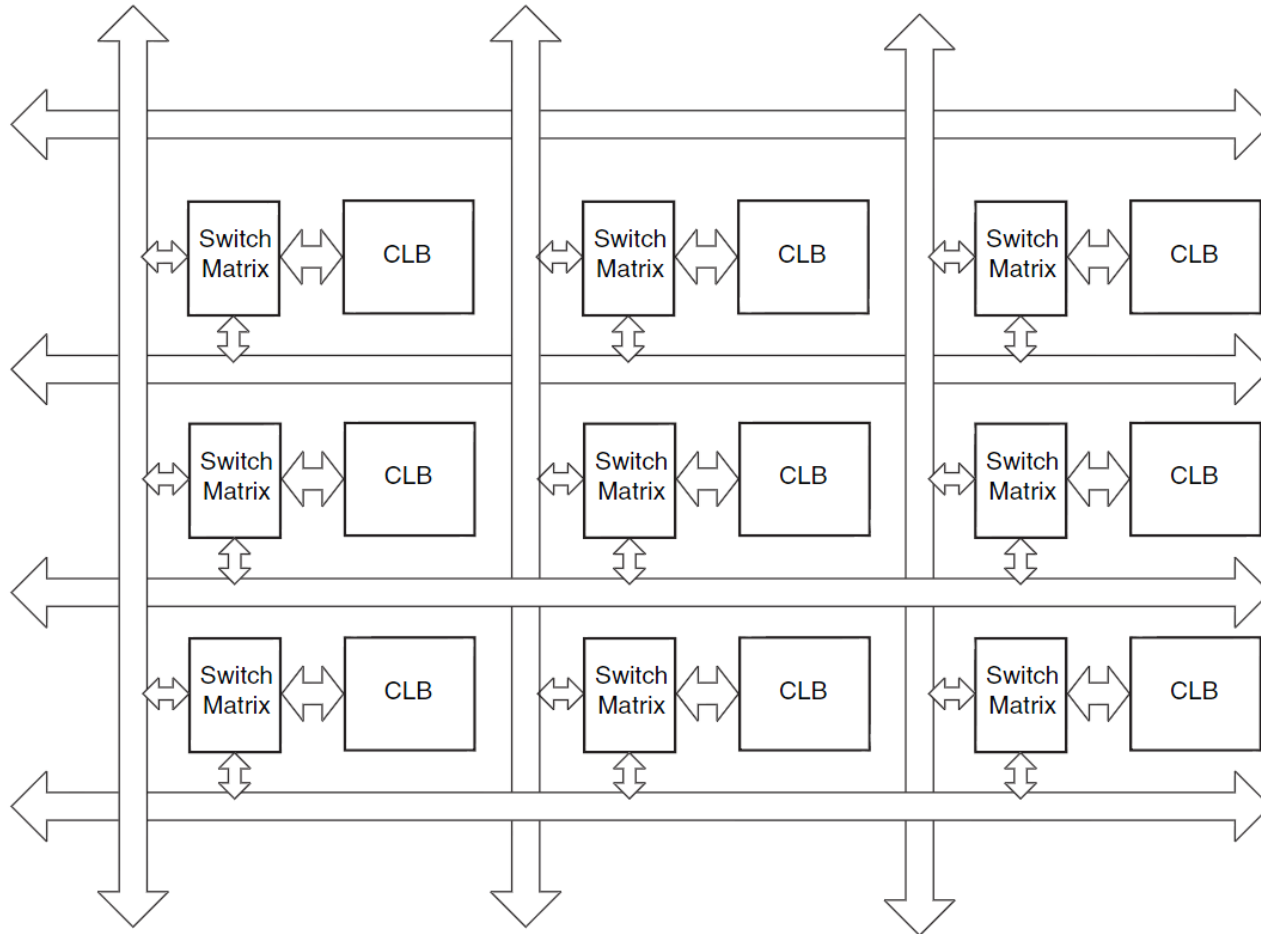


ug384\_29\_012710

Figure 29: CLB Array and Interconnect Channels
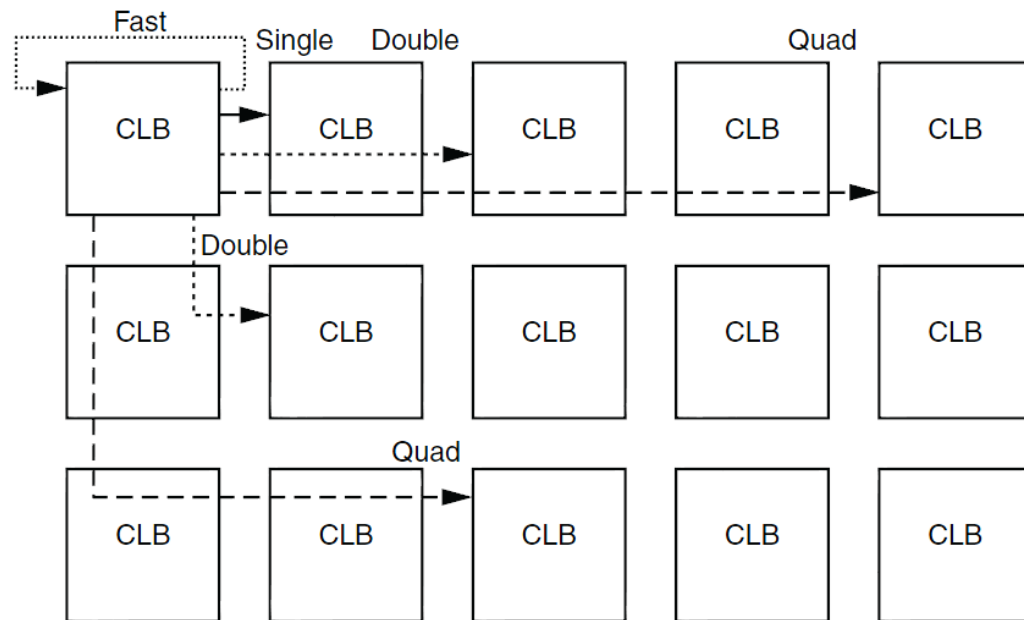
# FPGA internal layout

- Interconnect Distribution Network
  - Fast
  - Single
  - Double
  - Quad



UG384\_30\_012710


Figure 30: Examples of Interconnect Types



# FPGA internal layout

- Interconnect Distribution Network

- Fast
- Single
- Double
- Quad

 


# DESIGN GUIDELINES

# Overall design guidelines

- General principles and examples
- Throughput vs. Latency
- Timing

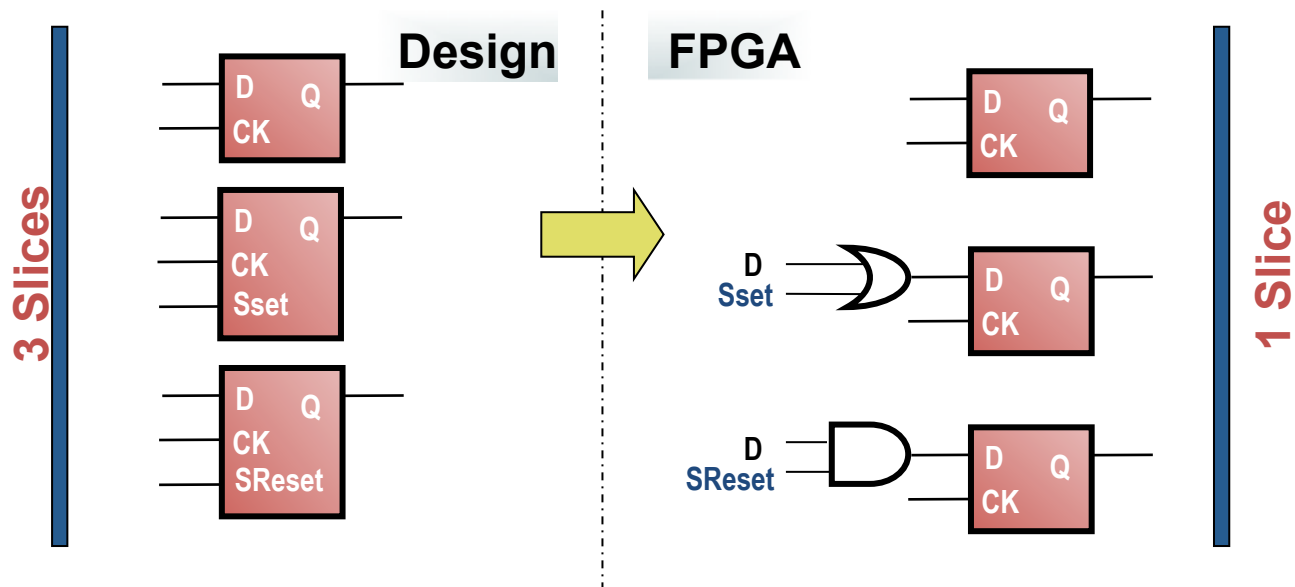
# Control Set Reduction

- Flip-flops with different control sets cannot be packed into the same slice
- Software can be instructed to reduce the number of control sets by mapping control logic to LUT resources
  - This results in higher LUT utilization, but a lower overall slice utilization


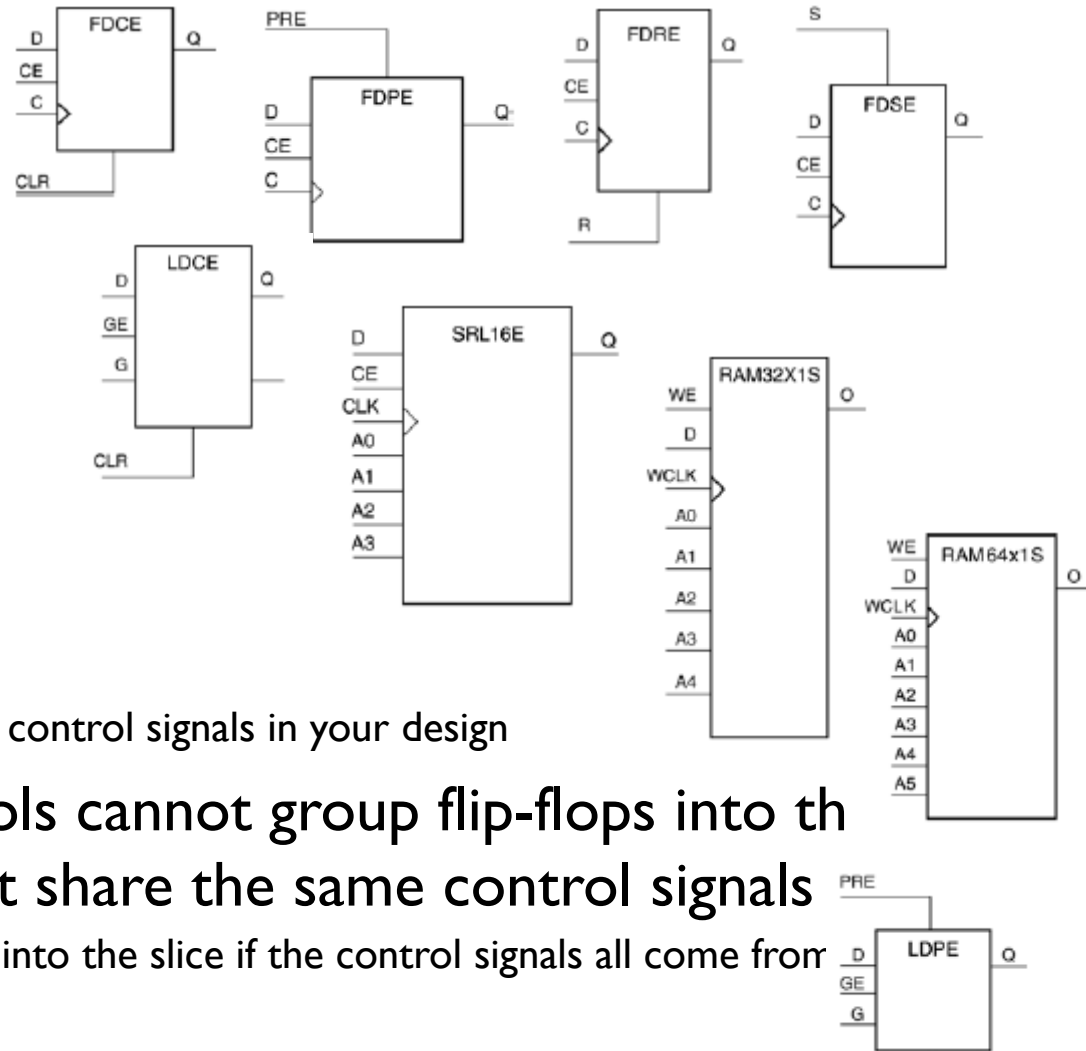
# Introduction to Control Sets

- A control signal is
  - Clock Enable / Gate Enable
  - Write Enable
  - Set / Reset
  - Preset / Clear
  - Clock / Gate
- A control set is
  - A group of enable, set, reset, and clock
- Unique control sets are
  - The number of groups of unique control signals in your design
- The implementation tools cannot group flip-flops into the same slice if they do not share the same control signals
  - However the tools can pack FFs into the slice if the control signals all come from set (next slide)



# Question

- Can these FFs be placed into the same slice (are they a part of the same control set)? (Note...all control signals drive the control port of the FF)
  - Case 1
    - FF1: CE, Set, Reset
    - FF2: Set, Reset
    - FF3: Reset
  - Case 2
    - FF1: CE, Set, Reset
    - FF2: Set2, Reset
  - Case 3
    - FF1: CE, Set, Reset
    - FF2: Set, not Reset

# Answer

## — Case 1...

- FF1: CE, Set, Reset
- FF2: Set, Reset
- FF3: Reset
- Yes! The tools can pack FFs into the slice if the control signals all come from the same set.

## — Case 2...

- FF1: CE, Set, Reset
- FF2: Set2, Reset
- No, two different sets cannot be grouped into the same slice. Same is true for CEs and the other control signals.

## — Case 3...

- FF1: CE, Set, Reset
- FF2: Set, not Reset
- Maybe, if the Reset is synchronous then your synthesis tool should be able to drive the reset to a LUT input and invert the reset signal.

- Note...if the control signal can be implemented as a LUT input (synchronous set, synchronous reset, or CE) then the tools have more flexibility to group those FFs into the same slice.

# Active-Low Control Signals

- Problem: Active-low control signals can produce sub-optimal results
- Why?
  - Control ports on registers are active-high
  - Hierarchical design and design re-use can propagate bad design practices
- This results in...
  - Poor device utilization
    - More LUTs
    - Less dense slice packing
    - More routing resources necessary
    - This requires additional inverters at all lower leaf levels
  - Longer run times
    - Prohibits hierarchical design flows (like incremental design)
    - More difficult timing
  - Worse timing and power

**Tip: Use active-high signals for CEs, sets, and resets**




# Overall design guidelines

- Think hardware
  - Create design block diagrams before coding
  - For all but really small designs implement the logic in small separate functional modules whenever it is possible
    - Easier to understand, implement and test
  - Build the complete design from the small, tested modules
  - I.e. structure your design using hierarchical design techniques
    - Simply instantiate your tested modules, configure and connect them.
    - Basically like doing object oriented SW development.
  - Use the RTL and Technology schematics to verify the design structure and inferred primitives


# Design Block Diagram Example

## ■ Unity-Link

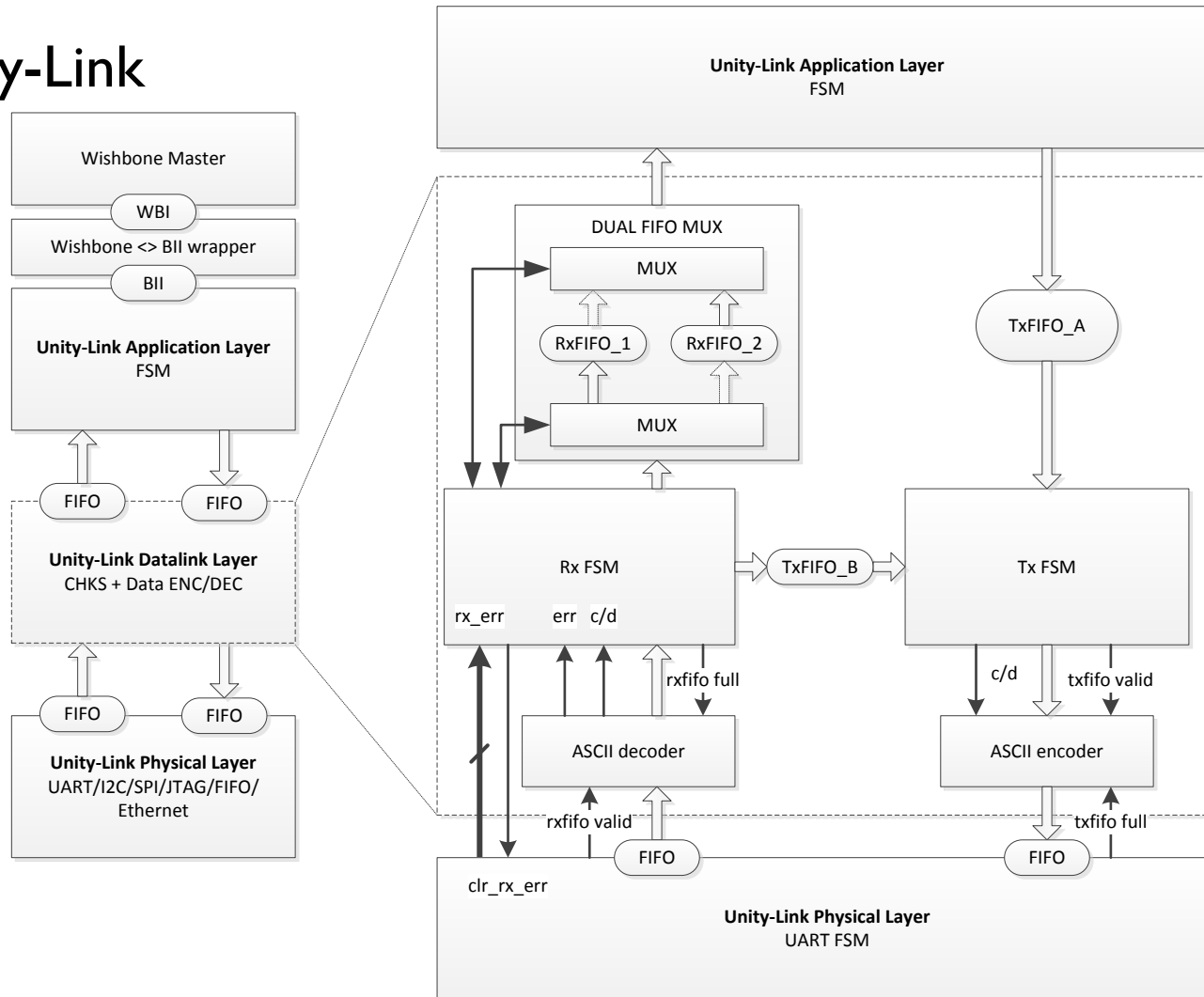


# Design Block Diagram Example

## ■ Unity-Link Datalink Layer RxFSM

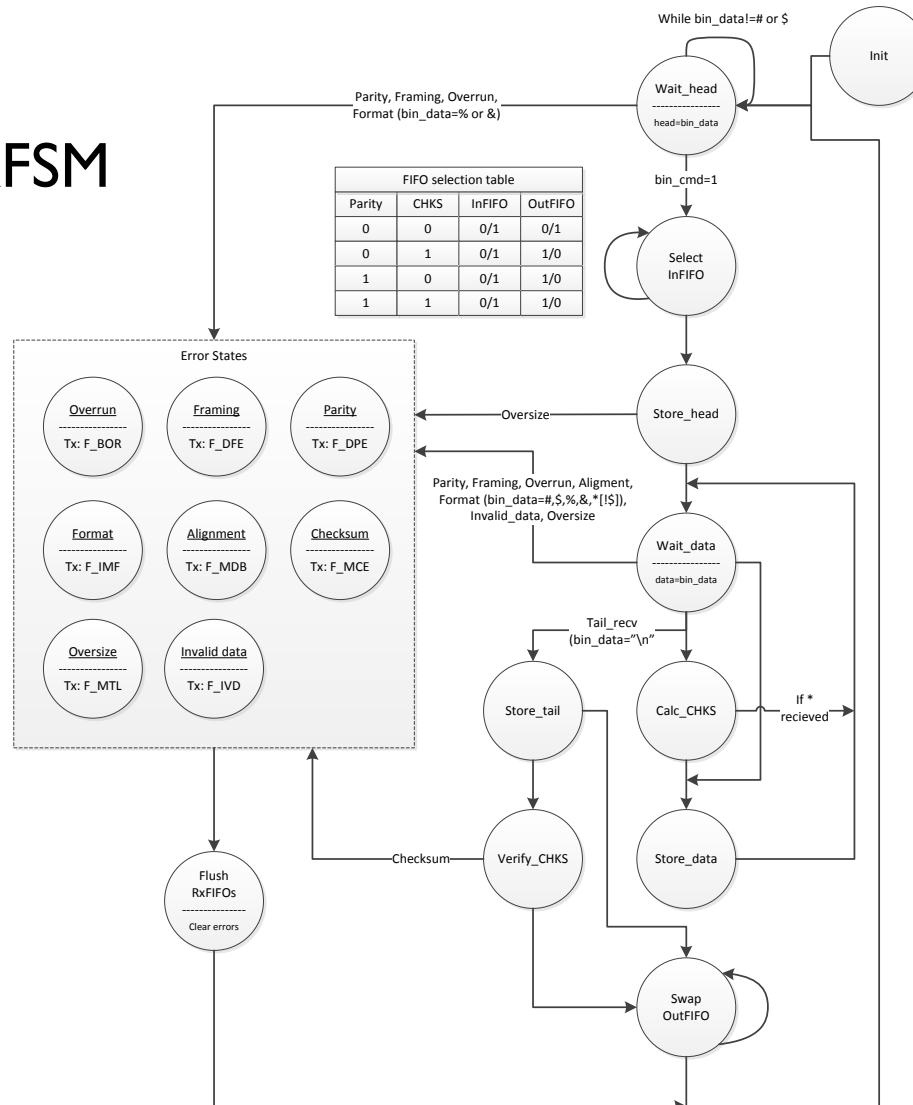

# Design Block Diagram example

## ■ Asynchronous FIFO

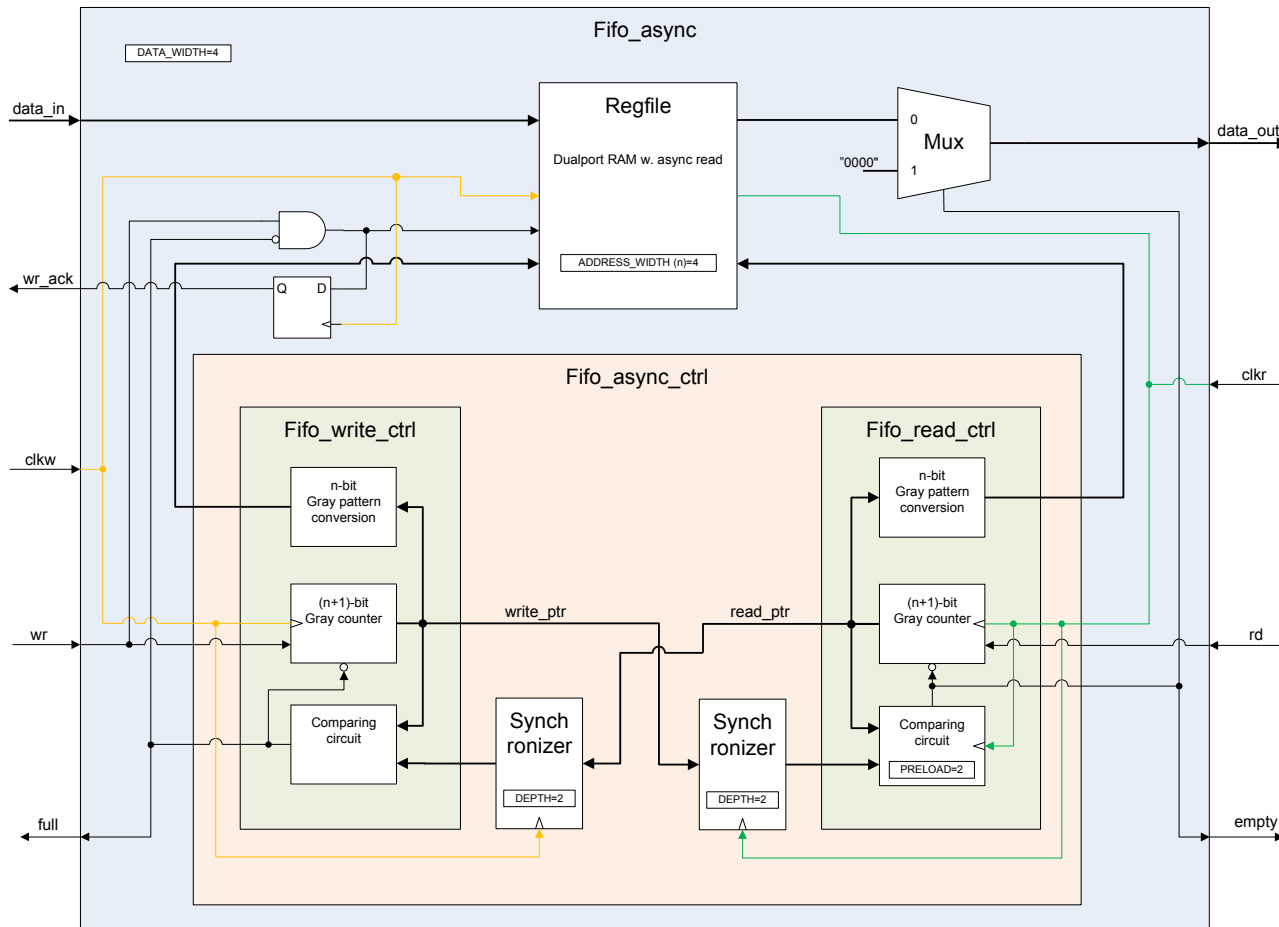


# Overall design guidelines

- Throughput vs. Latency
  - Throughput: *Number of bits in-/out-put per time-unit*
  - Latency: *Number of clocks before the output read reflects a given input.*

 
# Overall design guidelines

- Timing
  - Maximum frequency
  - Critical path
  - Automatic calculation


 
# Overall design guidelines

- Minimize critical path
  - Add register layers
  - Register balancing
  - Pipelining



# Overall design guidelines

- Throughput vs. Latency
- Example: (XC6LX45-3FG484)
  - Iterative (low area: 19 registers, 41 LUTs)
    - Throughput: 4 bits / 4 clocks = 1 bit / clock
    - Latency: 4 clocks
    - Critical path: One multiplier delay (3.325ns) => 288.976MHz
  - Low-Latency (low latency: 23 registers, 46 LUTs)
    - Throughput: 4 bits / clock
    - Latency: 2 clocks
    - Critical path: Two multiplier delays (3.565ns) => 280.493MHz
  - Pipelined (high throughput: 29 registers, 45 LUTs)
    - Throughput: 4 bits / clock
    - Latency: 3 clocks
    - Critical path: One multiplier delay (3.455ns) => 289.457MHz



# Synchronous designs

- Always make your design synchronous
  - Recommended for all FPGAs
- Failure to use synchronous design can potentially
  - Waste device resources
    - Not using a synchronous element will not save silicon and it wastes money
  - Waste performance
    - Reduces capability of end products; higher speed grades cost more
  - Lead to difficult design process
    - Difficult timing specifications and tool-effort levels
  - Cause long-term reliability issues
    - Probability, race conditions, temperature, and process effects
- Synchronous designs have
  - Few clocks
  - Synchronous resets
  - No gated clocks; instead, clock enables

# Synchronous designs

- RESET
  - Always use synchronous RESET (if at all possible)

**-- Flip-Flop with Positive Edge Clock  
-- and Asynchronous Reset VHDL  
-- Coding Example**

```
process (C, CLR)  
Begin  
    if (CLR = '1') then  
        Q <= '0';  
    elsif (C'event and C='1') then  
        Q <= D;  
    end if;  
end process;
```

**-- Flip-Flop with Positive Edge Clock and  
-- Synchronous Reset VHDL Coding  
-- Example**

```
process (C)  
begin  
    if (C'event and C='1') then  
        if (R='1') then  
            Q <= '0';  
        else  
            Q <= D;  
        end if;  
    end if;  
end process;
```

# FSM

```
1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY <entity_name> IS
6      PORT (clk, rst: IN STD_LOGIC;
7            input: IN <data_type>;
8            output: OUT <data_type>);
9  END <entity_name>;
10 -----
11 ARCHITECTURE <architecture_name> OF <entity_name> IS
12     TYPE state IS (A, B, C, ...);
13     SIGNAL pr_state, nx_state: state;
14     ATTRIBUTE ENUM_ENCODING: STRING; --optional attribute
15     ATTRIBUTE ENUM_ENCODING OF state: TYPE IS "sequential";
16 BEGIN
```

**#1 : Page 279-280**

# FSM

```
17  -----Lower section of FSM:-----  
18  PROCESS (clk, rst)  
19  BEGIN  
20      IF (rst='1') THEN  
21          pr_state <= A;  
22      ELSIF (clk'EVENT AND clk='1') THEN  
23          pr_state <= nx_state;  
24      END IF;  
25  END PROCESS;
```

```

26  -----Upper section of FSM:-----
27  PROCESS (pr_state, input)
28  BEGIN
29      CASE pr_state IS
30          WHEN A =>
31              output <= <value>;
32              IF (input=<value>) THEN
33                  nx_state <= B;
34                  ...
35              ELSE
36                  nx_state <= A;
37              END IF;
38          WHEN B =>
39              output <= <value>;
40              IF (input=<value>) THEN
41                  nx_state <= C;
42                  ...
43              ELSE
44                  nx_state <= B;
45              END IF;

```

**#1 : Page 279-280**

```


42         ...
43         ELSE
44             nx_state <= B;
45         END IF;
46     WHEN ...
47     END CASE;
48 END PROCESS;
49 -----Output section (optional):-----
50 PROCESS (clk, rst)
51 BEGIN
52     IF (rst='1') THEN
53         new_output <= <value>;
54     ELSIF (clk'EVENT AND clk='1') THEN --or clk='0'
55         new_output <= output;
56     END IF;
57 END PROCESS;
58 END <architecture_name>;
59 -----

```

## #1 : Page 279-280
 
# RESET

- RESET
  - Never use global RESET (if a all possible)



WP272\_02\_010708

**Figure 2: Reset Timing Diagram - Asserted Asynchronously to the Clock**

# Feedback on exercise from last week




# Exercise

- Exercise
  - Sliding average filter
    - Understand what is happening
      - Note the use of a variable! (*sum*)
      - Simulate if necessary

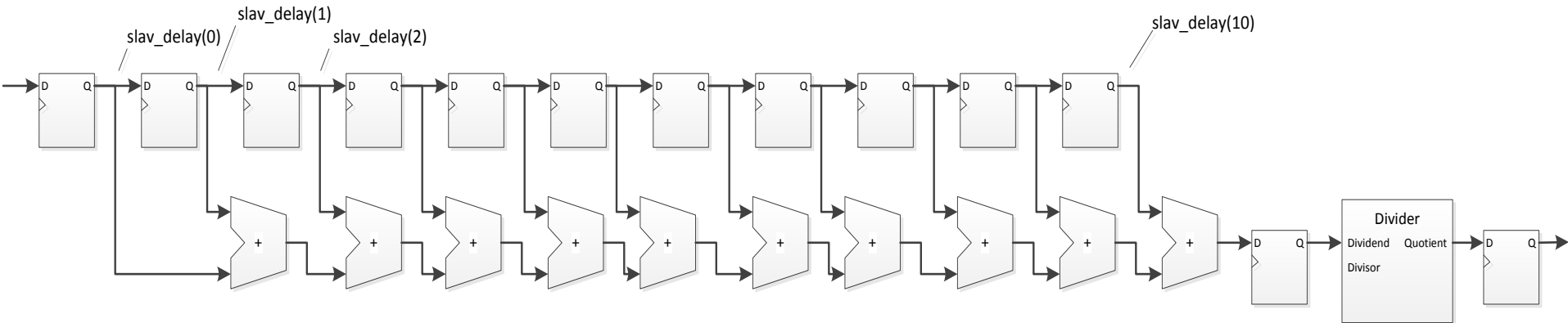
# Exercise

- Sliding Average Filter
  - Divisor = 11


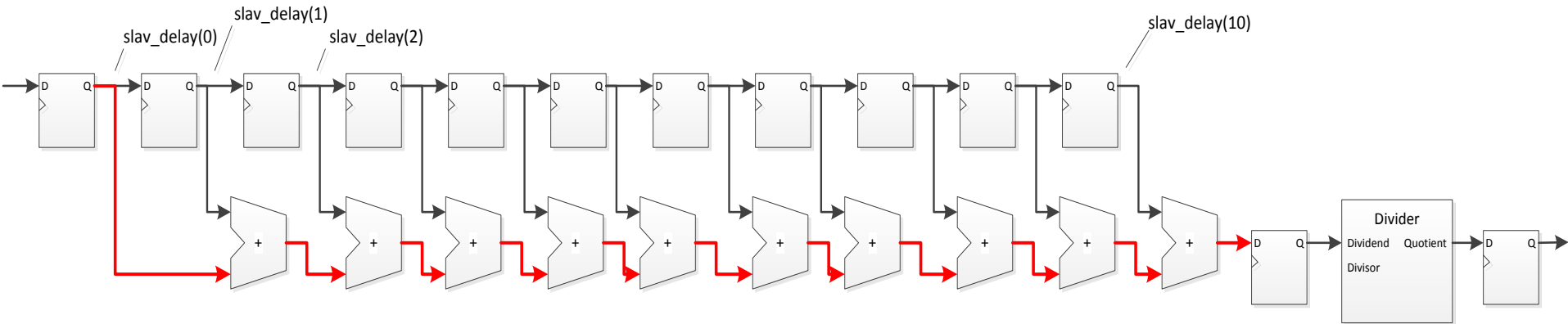
# Exercise

- Sliding Average Filter
  - Divisor = 11




# Exercise

- Exercise
  - Sliding average filter
    - Understand what is happening
      - Note the use of a variable! (*sum*)
      - Simulate if necessary
    - Improve the filter! (Target frequency: +400 MHz)
      - Original data:
        - Slice count: 87
        - Slice Register count: 475 (MAP: 404)
        - Slice LUT count: 214 (MAP: 270)
        - Maximum frequency: 147.009 MHz
        - Latency: 19 clock periods
  - Save your files for next week!

# Exercise
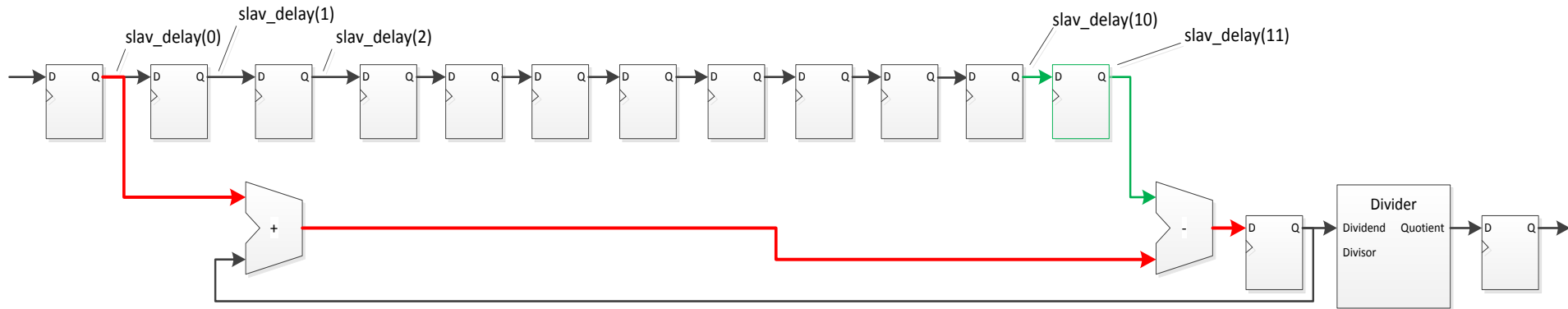
## ■ Improved Sliding Average Filter (Divisor = 11)



### ■ Original Filter data:

- Slice count: 87
- Slice Register count: 475 (MAP: 404)
- Slice LUT count: 214 (MAP: 270)
- Maximum frequency: 147.009 MHz
- Latency: 19 clock periods


### ■ Improved Filter Data:

- Slice count: 75
- Slice Register count: 424 (MAP: 318)
- Slice LUT count: 145 (MAP: 206)
- Maximum frequency: 409.752MHz
- Latency: 19 clock periods

# Exercise

- Alternative Sliding Average Filter using FPGA primitives

- Divisor = 16

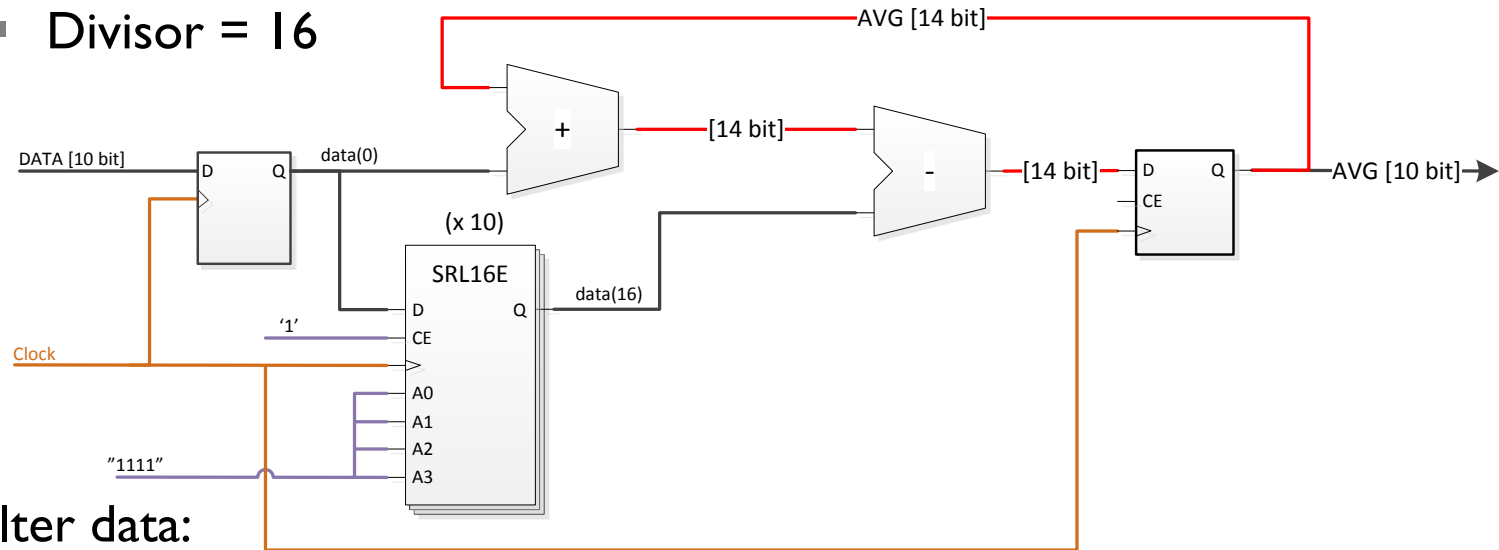

- Filter data:

- Slice count: 10
  - Slice Register count: 24
  - Slice LUT count: 34 (MAP: 32)
  - Maximum frequency: 251.946MHz
  - Latency: 2 clock periods

# Task for next lesson

- Read ALL the mandatory material:
  - See BlackBoard (From Monday)
- Work on / Update your blockdiagram, detailing:
  - All top level-modules/functions and their relationship (connections)
  - Module connections must be detailed signal and bus lines, simple data-flow descriptions are not enough.
  - Remember that the ADCs delay the R, G and B color signals relative to the H, and V sync signals...
    - Figure out how much the R, G and B signals are delayed
    - Compensate for this delay, to ensure the H -and V-sync signal are in sync with the color lines.
- Group status presentation (5 minutes pr. group)